

Signal Filtering - Medium Problem

Written by: Joshua Beard (jbeard5@uw.edu)

You are designing a radio telemetry circuit, and want to receive signals specifically on 500MHz. You can assume you already have the input signal from the antenna (it is a sum of many sine waves of many different frequencies).

Build a circuit that takes this signal as an input and results in only the sine wave at 500MHz. It is acceptable to let through a small amount of signals on each side of 500MHz, but justify and quantify these inaccuracies.