

LED Supply - Easy Problem

Written by: Joshua Beard (jbeard5@uw.edu)

You are designing a circuit to power an LED, but you have encountered an issue. Strangely, the only power signal you have access to is a square wave. It is 5V for 100ms, and 0V for 100ms, repeating. You want the LED to always be on, but as is, the LED is turning on and off at a frequency of 5hz. This is definitely not what you want.

Design a circuit that takes the square wave as an input and powers the LED in a way so it stays continuously lit.